

EELE 250: Circuits, Devices, and Motors

Lecture 11

Assignment Reminder

- Read 4.1 - 4.3 AND 5.1 - 5.4
- Practice Problems:
 - P3.60, 3.64, 3.72
 - P4.3, 4.8, 4.9, 4.23, 4.37, 4.38
- D2L Quiz #5 by 11AM on Monday 30 Sept.
- Lab #4 will be performed next—be sure to do the pre-lab assignment calculations!

Sinusoidal Current and Voltage

- $v(t) = V_m \cos(\omega t + \theta)$
- $\omega = 2 \pi f$ [radians / sec]
- $f =$ frequency [cycles / sec] or [Hz]
- $T = 1 / f =$ period [sec]
- Root mean square (RMS) concept

Sinusoids

- Which is the correct relationship between sine and cosine?
 - A. $\cos(\theta) = \sin(\theta + \pi/2)$
 - B. $\cos(\theta) = \sin(\theta - \pi/2)$
 - C. $\cos(\theta) = \sin(\theta + \pi)$
 - D. $\cos(\theta) = \sin(\theta - \pi)$
 - E. $\cos(\theta) = -\sin(\theta)$


Sinusoids

- Which is the correct relationship between sine and cosine?
 - A. $\sin(\theta) = -\cos(\theta)$
 - B. $\sin(\theta) = \cos(\theta + \pi/2)$
 - C. $\sin(\theta) = \cos(\theta - \pi)$
 - D. $\sin(\theta) = \cos(\theta - \pi/2)$
 - E. $\sin(\theta) = \cos(\theta + \pi)$

Phasors

- Represent a sinusoid $v(t) = V_1 \cos(\omega t + \theta_1)$ as a vector of length V_1 and angle θ_1 with respect to the real axis
- This vector is equivalent to a *complex number*
real part is $V_1 \cos(\theta_1)$
and
imaginary part is $V_1 \sin(\theta_1)$
- (Polar form vs. rectangular form)

Phasors (cont.)

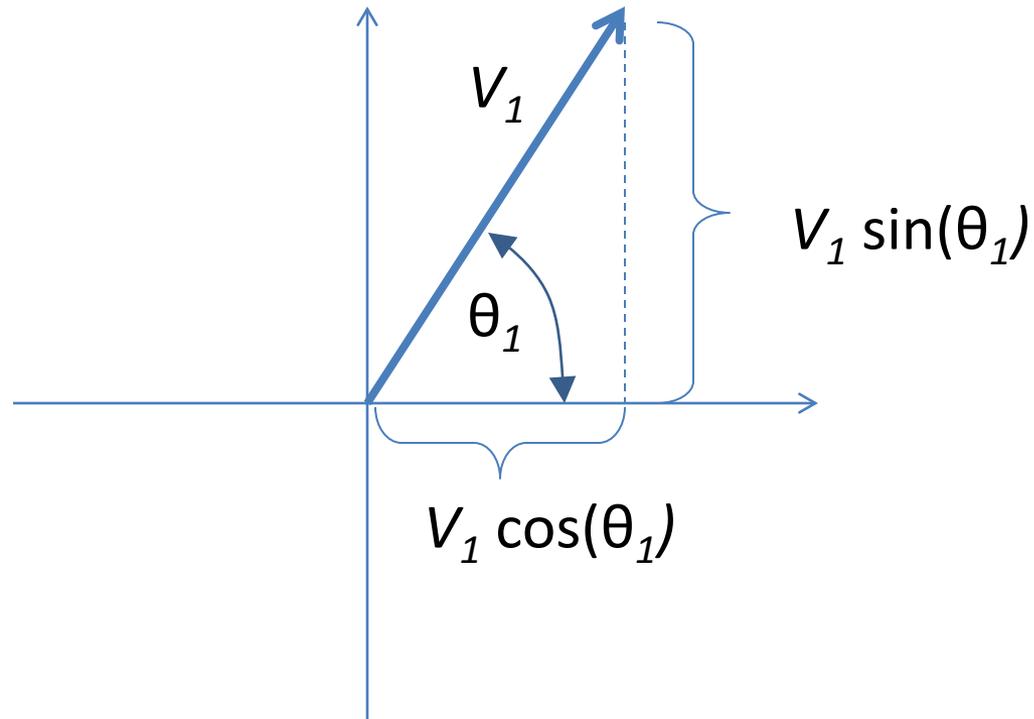

Phasors (cont.)

- Circuits with sinusoidal signals often result in KVL or KCL expressions like:

$$V_1 \cos(\omega t + \theta_1) + V_2 \cos(\omega t + \theta_2) + V_3 \cos(\omega t + \theta_3)$$

It is a pain to add these signals via trigonometric identities!

Fortunately, it is easier to add using phasors: add the vectors as complex numbers.

Phasors (cont.)

$$V_1 \cos(\omega t + \theta_1) + V_2 \cos(\omega t + \theta_2) + V_3 \cos(\omega t + \theta_3)$$

Phasors: $V_1 \angle \theta_1 + V_2 \angle \theta_2 + V_3 \angle \theta_3$

Real parts: $V_1 \cos(\theta_1) + V_2 \cos(\theta_2) + V_3 \cos(\theta_3)$

Imag parts: $V_1 \sin(\theta_1) + V_2 \sin(\theta_2) + V_3 \sin(\theta_3)$

Sum phasor:

$$\text{sqrt}(\text{real}^2 + \text{imag}^2) \angle \text{atan}(\text{imag}/\text{real})$$

Complex impedances

- Inductor: $v(t) = L \, di/dt$
- If $i(t) = I_m \cos(\omega t)$, then $v(t) = -\omega I_m L \sin(\omega t)$
 \Rightarrow note that $-\sin(\omega t) = \cos(\omega t + 90^\circ)$

- As phasors:

$$I = I_m \angle 0^\circ \qquad V = \omega I_m L \angle 90^\circ$$

which means:

$$V = (\omega L \angle 90^\circ) \cdot (I)$$

Note: $\omega L \angle 90^\circ$ is the complex number $j \omega L$

Complex Impedances (cont.)

- $V = (\omega L \angle 90^\circ) \cdot (I) = (j \omega L) \cdot (I)$
- Ohm's Law: $V = I \cdot R$, can be generalized to

$V = I \cdot Z$, where Z is the *impedance*.

- Z can be a real or a complex number
 - Impedance of a resistor: $Z = R$
 - Impedance of an inductor: $Z = j \omega L$
 - Impedance of a capacitor: $Z = 1/(j \omega C)$

Complex Impedances (cont.)

- NOTE that the impedance of an inductor or capacitor depends upon the sinusoidal frequency, ω

$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$

- Impedance magnitude of inductor goes *up* as frequency increases
- Impedance magnitude of capacitor goes *down* as frequency increases

Summary and Review

- Represent a group of sinusoids with the same frequency as *phasors*
- Add phasors by interpreting them as complex numbers
- Generalize Ohm's Law to be $\mathbf{V} = \mathbf{I} \mathbf{Z}$
- Impedance of a resistor: $\mathbf{Z} = R$
- Impedance of an inductor: $\mathbf{Z} = j \omega L$
- Impedance of a capacitor: $\mathbf{Z} = 1/(j \omega C)$