


EELE 250: Circuits, Devices, and Motors

Op Amps (cont.)


Assignment Reminder

- Read 14.4 - 14.7
- Practice Problems:
 - P14.19, P14.20, P14.22, P14.23, P14.32
- Lab #7 next week. Note that there is a design to be done in the prelab.
- NO D2L Quiz this weekend
- Exam #3: Friday 15 Nov.


Non-Inverting amplifier

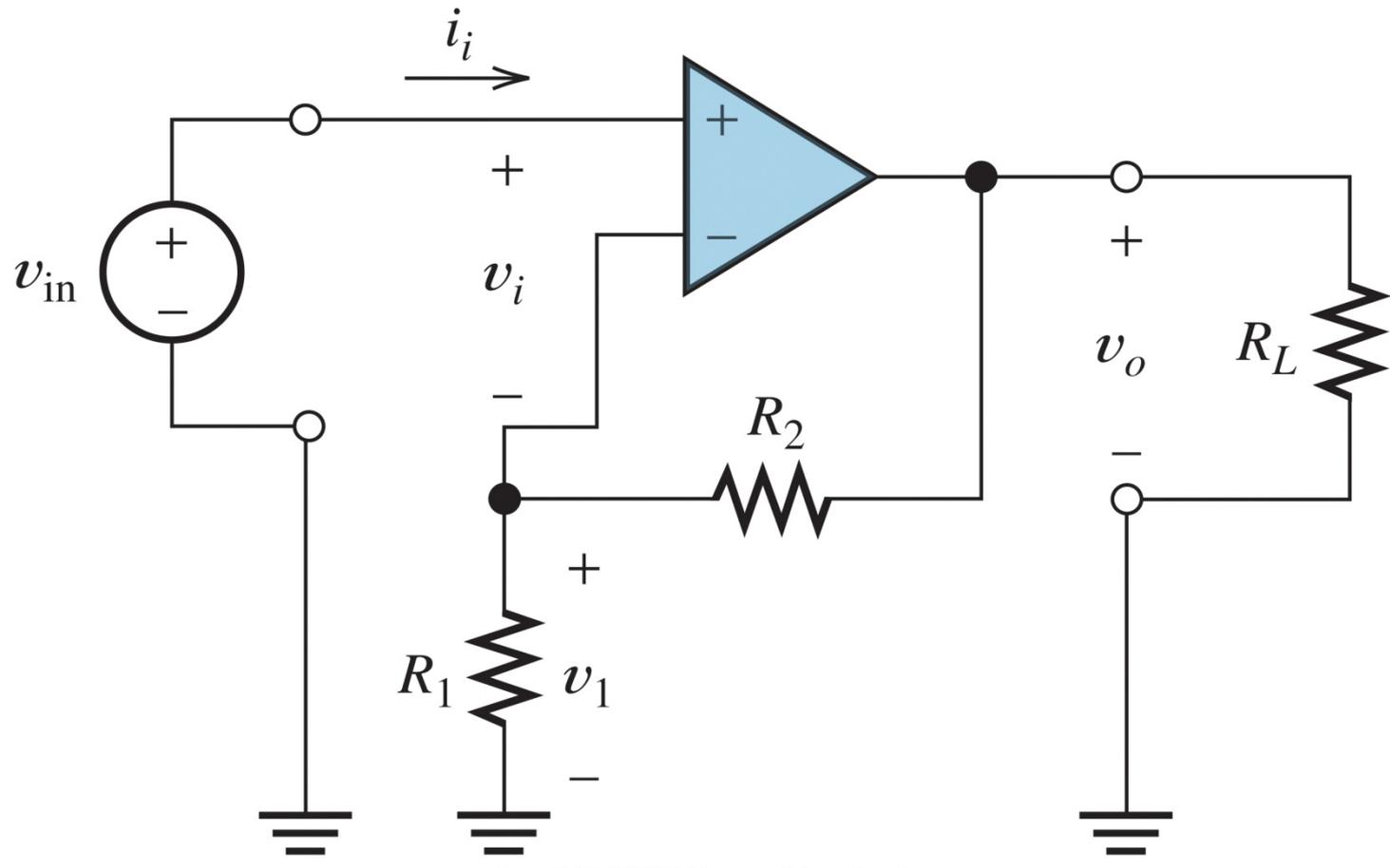

Inverting Summer

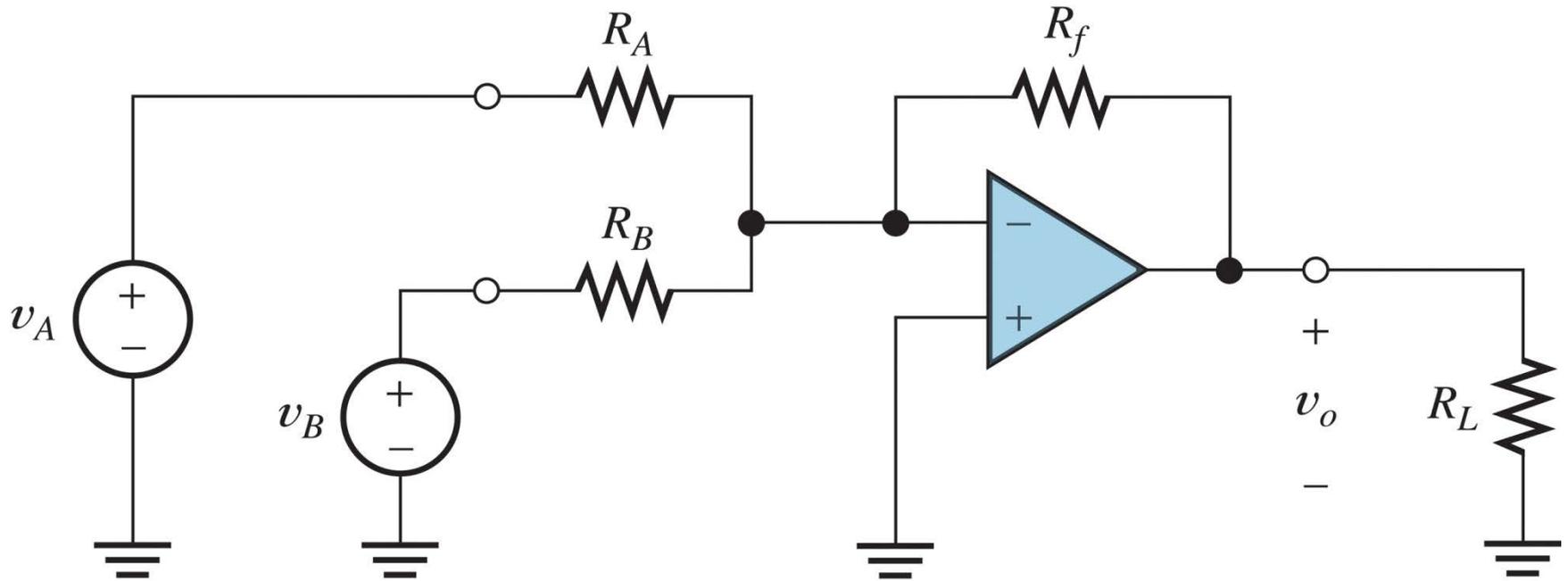

Differential amplifier

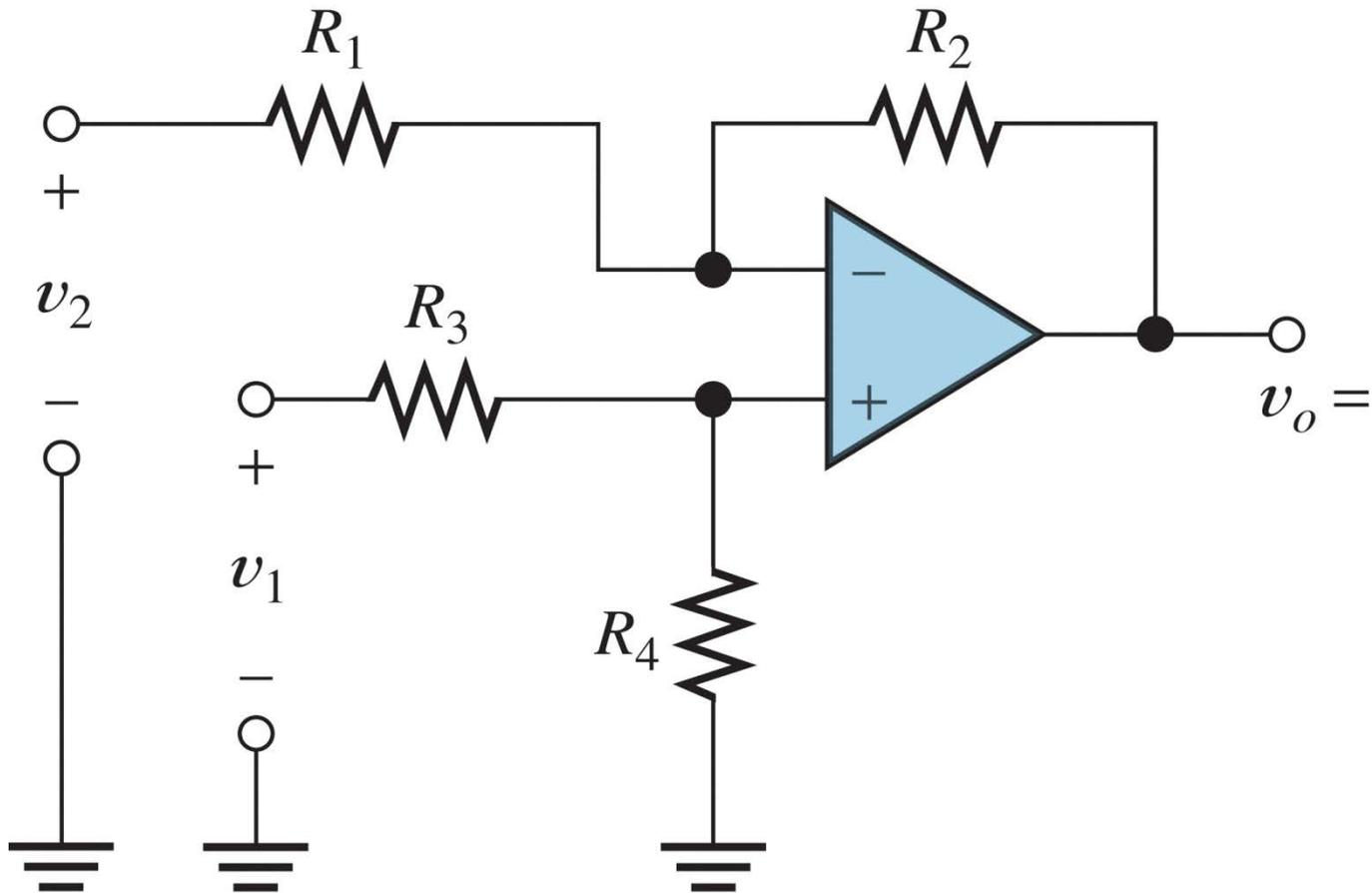

Differentiator

