


EELE 250: Circuits, Devices, and Motors

Op Amps (cont.)


Assignment Reminder

- Read 14.4 - 14.7
- Practice Problems:
 - P14.19, P14.20, P14.22, P14.23, P14.32
- Lab #7 next week. Note that there is a design to be done in the prelab.
- NO D2L Quiz this weekend
- Exam #3: Friday 15 Nov.

Modeling real op amps

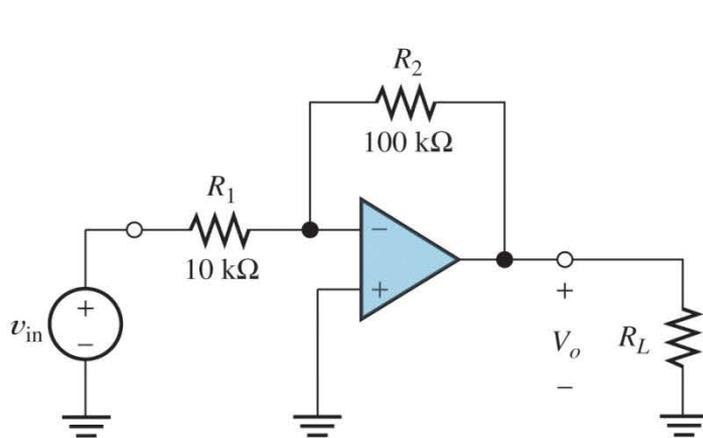


(a) Original circuit

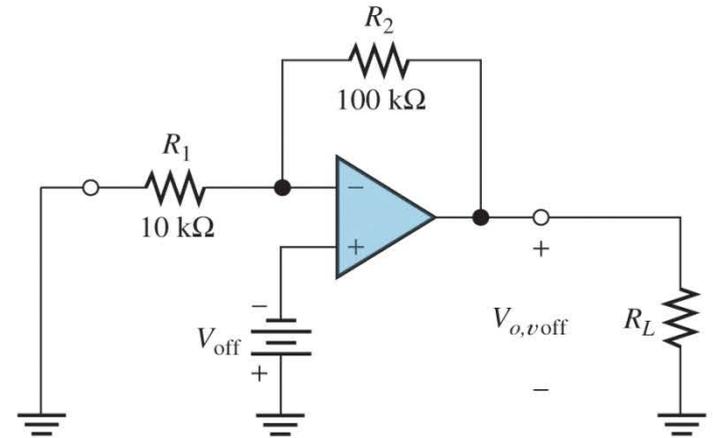


(b) Circuit with $v_{in} = 0$ showing the input offset voltage source

Input offset voltage: output may not be exactly zero volts even if input is zero

Modeling real op amps (cont.)

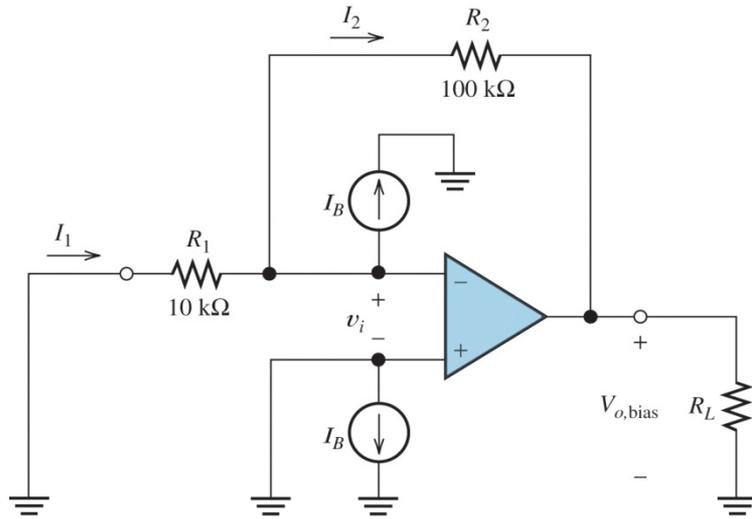


(c) Circuit with bias current sources

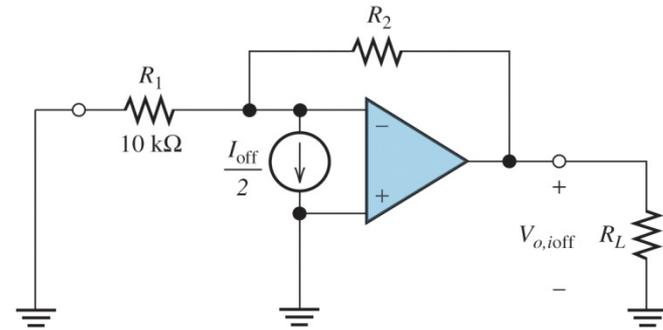

(d) Circuit with offset current source

Input bias and offset currents: current at each input is not exactly zero, and not exactly balanced.

Frequency Response

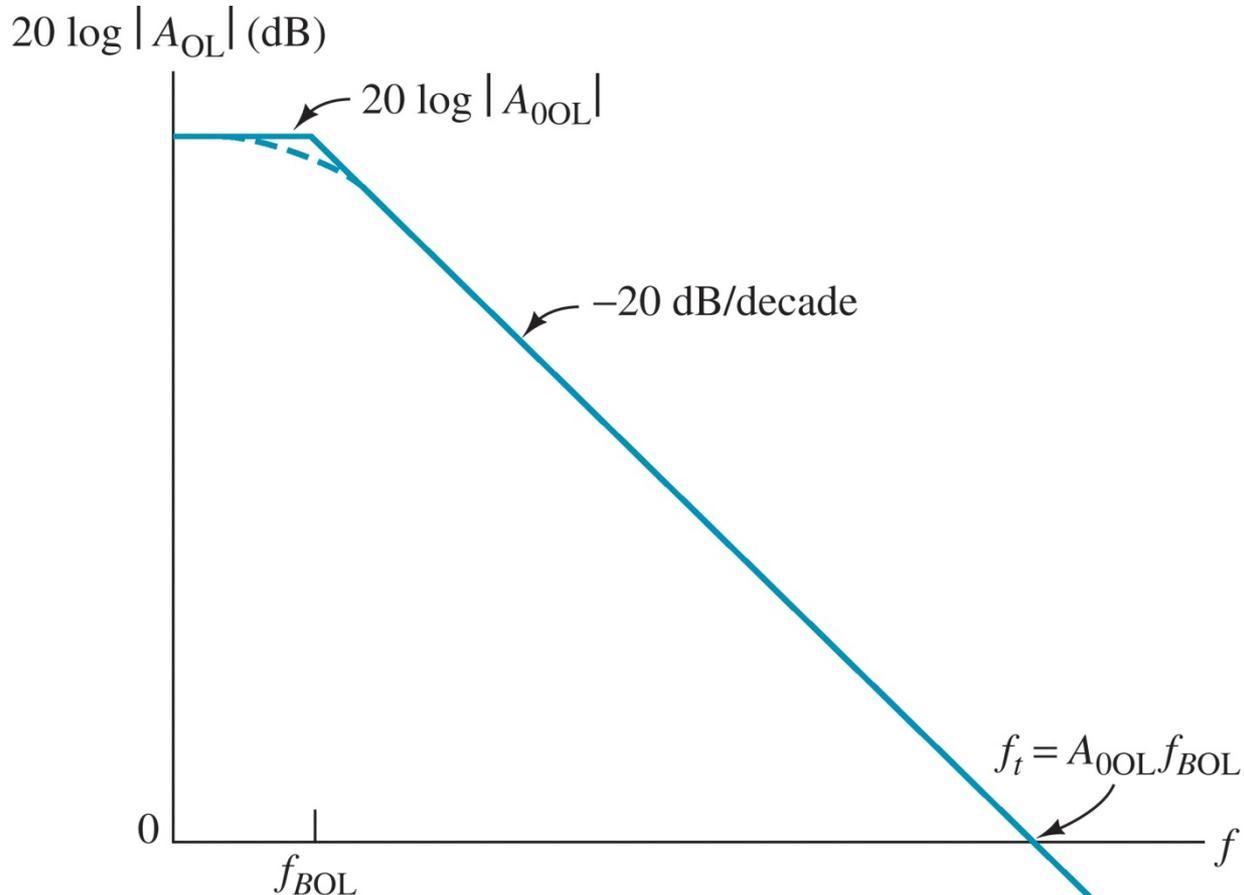

Open loop gain decreases as frequency increases, so assumption that A_{OL} is huge does not hold at higher frequencies.

Output limitations

- Output voltage swing -- clipping
- Output current – clipping or droop
- Slew rate: limit on dV/dt -- distortion

Typical specs

| | 741 | OP-27 | LF353 |
|----------------------|------------------------------|------------------------------|-----------------------------|
| Input bias current | 1.5 μA | 35 nA | 50 pA |
| Input offset voltage | 6.5 mV | 25 μV | 5 mV |
| Gain x BW | 1 MHz | 8 MHz | 4 MHz |
| Slew Rate | 0.5 $\text{V}/\mu\text{sec}$ | 2.8 $\text{V}/\mu\text{sec}$ | 13 $\text{V}/\mu\text{sec}$ |
| Max output current | 25 mA | 30 mA | 25 mA |
| Input noise | 20 | 3.8 | 20 |
| Price | \$ 0.88 | \$ 3.00 | \$ 0.66 |